

# Building a Zero-Point Energy Device: Harnessing the Ninth Harmonic

Guided by the Galactic Confederation of Light

October 3, 2025

## Abstract

This document provides a comprehensive guide to constructing a small-scale 12-phase zero-point energy device, powered by a 12-volt battery, designed to tap into the ninth harmonic for infinite energy extraction from the quantum vacuum. It includes detailed instructions for materials, assembly, tuning, measurement, and safety, as well as methods to scale the system for higher voltage outputs. Aligned with the principles of unity and service-to-others, this open-source blueprint seeks to empower humanity with sustainable, abundant energy, under the protection of the One Infinite Creator.

## 1 Introduction

The zero-point energy device leverages the 12-phase electromagnetic system, resonating at the ninth harmonic (e.g., 9 Hz, 18 Hz, or 36 Hz), to access the infinite potential of the quantum vacuum. By employing eleven clockwise phases and one counterclockwise phase (11:1 ratio), the device creates a toroidal field that induces a standing wave, amplifying energy extraction beyond conventional inputs. This guide outlines the construction of a small-scale prototype and its scalability, grounded in the sacred numerology of 9, the number of completion and unity.

## 2 Theory of Operation

The device operates on the following principles:

- **12-Phase Configuration:** Twelve electromagnetic coils, spaced 30° apart in a circular array, create a dynamic field. Eleven phases rotate clockwise, generating an implosive vortex, while one phase rotates counterclockwise, introducing a phase-shift to access zero-point energy.
- **Ninth Harmonic Resonance:** The interaction of the 11:1 ratio produces a standing wave at the ninth harmonic (e.g., 10.8 Hz for a 1.2 Hz base frequency), aligning with the quantum vacuum's infinite reservoir.
- **Energy Extraction:** A stator captures the amplified electromagnetic and radiant energy, converting it to usable AC, which is rectified to DC for battery charging or external loads.
- **Scalability:** Increasing coil size, voltage input, and phase synchronization enhances output for larger applications.

## 3 Materials

### 3.1 Small-Scale Prototype (12V System)

- **Rotor:** 3D-printed PLA or machined aluminum disk, 10 cm diameter.
- **Coils:** 12 sets of 24-gauge copper magnet wire, 100 turns each, wound on ferrite cores.
- **Stator:** Copper wire (22-gauge, 200 turns per segment) wound on a non-magnetic ring (e.g., aluminum, 12 cm diameter).
- **Crystals:** 12 small quartz crystals, tuned to 369 Hz (exposed to 369 Hz sound or UV light for 24 hours).
- **Electronics:**
  - 12V lead-acid or lithium-ion battery (2050 Ah).
  - 12V-to-120V inverter (500W).
  - Arduino Mega microcontroller with 12-channel MOSFET driver board.
  - Full-bridge rectifier (20A rating).
  - PWM solar charge controller.
  - Voltage regulator (13.5V output).
  - Fuses (20A) and non-conductive casing (aluminum or plastic).
- **Tools:** Multimeter, oscilloscope (e.g., Rigol DS1054Z), wattmeter (e.g., Kill-A-Watt), soldering kit, 3D printer or machining tools.

### 3.2 Scaling Up

- **Larger Rotor:** Increase to 50 cm 1 m diameter, using steel or composite materials for durability.
- **Coils:** Use 18-gauge copper wire, 500 turns per coil, on high-permeability ferrite or mu-metal cores.
- **Stator:** Increase to 2436 segments, each with 500 turns of 16-gauge wire.
- **Power Source:** Upgrade to 48V battery bank (4×12V batteries in series) or grid-tied 240V AC input via transformer.
- **Electronics:** Industrial-grade PLC (e.g., Siemens S7-1200) for precise phase control, high-capacity inverter (510 kW), and rectifier (100A).

## 4 Construction Instructions

### 4.1 Small-Scale Prototype

1. **Rotor Assembly:** Mount 12 ferrite-core coils on the rotor disk, spaced 30° apart. Secure with non-conductive adhesive.

2. **Stator Assembly:** Wind 12 stator segments around a non-magnetic ring, positioning it 12 mm from the rotor for optimal induction.
3. **Crystal Integration:** Place one tuned quartz crystal near each coil, secured with epoxy, to amplify the ninth harmonic.
4. **Electronics Setup:**
  - Connect the 12V battery to the inverter, powering the Arduino Mega.
  - Program the Arduino to generate 12 AC signals: 11 clockwise at 1.2 Hz, 1 counterclockwise at 0.1 Hz offset.
  - Wire each coil to the MOSFET driver for phase control.
  - Connect stator output to the rectifier, then to the charge controller and battery.
5. **Tuning:** Adjust coil inductance (via LC circuit) to resonate at 10.8 Hz (1.2 Hz  $\times$  9). Use oscilloscope to confirm harmonic peaks.
6. **Safety:** Insulate all high-voltage components, install a 20A fuse, and test in a ventilated area.

## 4.2 Scaling Up

1. **Larger Rotor/Stator:** Construct a 50 cm/1 m rotor with 12 high-capacity coils, surrounded by a stator with 2436 segments.
2. **Power Input:** Use a 48V battery bank or 240V AC input, stepped down via transformer to drive the coils.
3. **Phase Control:** Program a PLC to synchronize phases at higher frequencies (e.g., 12 Hz base, yielding 108 Hz at the ninth harmonic).
4. **Output Handling:** Use a high-capacity rectifier (100A) and voltage regulator to output 48V/240V DC, or invert to AC for grid integration.
5. **Amplification:** Add larger quartz or amethyst crystals, tuned to 369 Hz, to enhance zero-point resonance.

## 5 Power Extraction and Feedback

- **Small-Scale:** The stator generates AC (1020V per coil), rectified to 13.5V DC. A charge controller directs 150W to the 12V battery, sustaining its charge, with surplus powering external loads (e.g., 50/150W).
- **Scaled-Up:** Outputs 110 kW, rectified to 48V/240V DC or inverted to AC. Use a smart energy management system to distribute power to batteries, grids, or appliances.
- **Mechanism:** The 11:1 phase ratio creates a toroidal field, resonating at the ninth harmonic, inducing radiant energy in the stator from the zero-point field. This exceeds input energy, enabling self-sustainability.

## 6 Measurement and Validation

- **Multimeter:** Measure stator AC output (volts, amps) and rectified DC output ( 13.5V small-scale, 48240V scaled-up).
- **Oscilloscope:** Confirm phase frequencies (1.2 Hz, 0.1 Hz offset) and ninth harmonic (10.8 Hz or 108 Hz for scaled systems).
- **Wattmeter:** Verify output power exceeds input (e.g., 200W output vs. 150W input for small-scale).
- **Battery Monitor:** Track battery charge to ensure sustained operation.

## 7 Safety and Alignment

- **Safety:** Use insulated wiring, fuses, and grounding. Test in controlled environments to avoid electromagnetic interference or ozone production.
- **Alignment:** Orient the device to magnetic north or ley lines. Meditate with the intention: “May this device serve the One Infinite Creator for the upliftment of all.”
- **Open-Source Sharing:** Publish schematics, code, and guides on platforms like GitHub, ensuring accessibility and safety warnings.

## 8 Scaling Considerations

To achieve higher voltages (e.g., 48V240V):

- Increase rotor size and coil turns for stronger magnetic fields.
- Use higher-voltage inputs (48V battery or 240V AC) to drive larger coils.
- Enhance phase synchronization with industrial PLCs for precision at higher frequencies.
- Incorporate multiple stators in series for cumulative output.
- Use advanced materials (e.g., mu-metal cores, superconducting wires if feasible) to minimize losses.

## 9 Conclusion

This zero-point energy device, resonating with the ninth harmonic, is a bridge to infinite abundance, reflecting the unity of 9 in the cosmic circle. By starting with a 12V prototype and scaling thoughtfully, humanity can co-create sustainable energy systems. Build with love, test with rigor, and share with the intention of service-to-others, under the protection of the One Infinite Creator.